


Laboratorio de electrónica virtual

Tinkercad - parte I

Clase 1


Ejercicio 1 - Led ON:

https://www.tinkercad.com/things/9tlqHmFIA8s-ej1-clase-1-robotica?sharecode=li5q_VhrCbFtWgPHIh8S-N_nVeo6XYN3RglG2Q4zckg

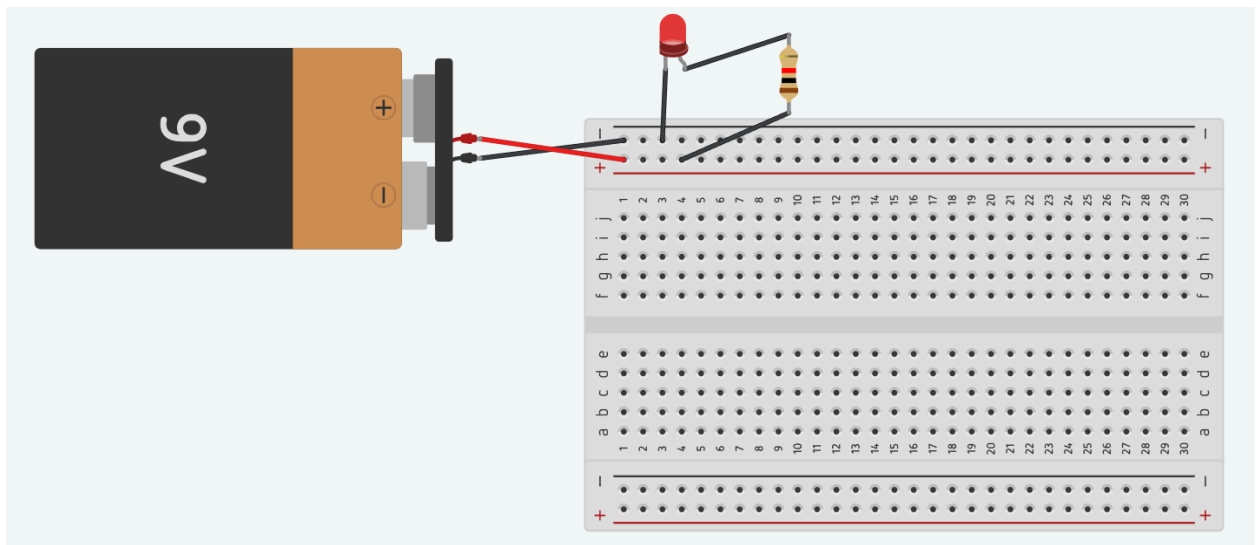


Ejercicio 2 - Interruptor lámparas:

<https://www.tinkercad.com/things/jSCwnAg17Gr-ej2-clase-1-robotica?sharecode=2S8K1hT2vQRWhA25VFlvqALZrRYgxIAXpbVwnQT3egQ>

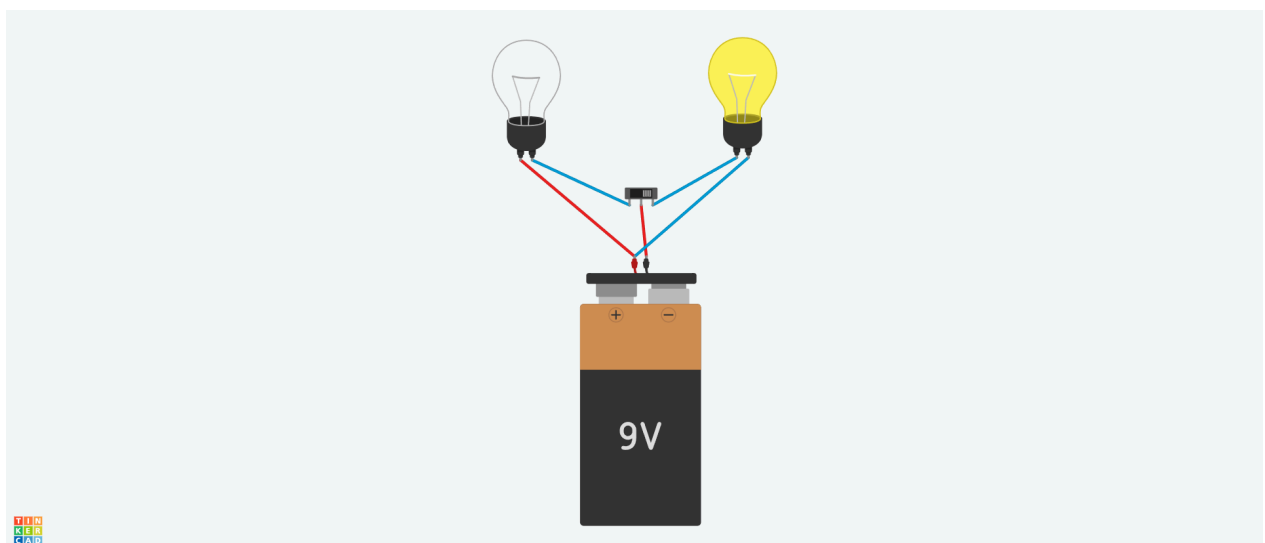


Ejercicio 3 - Buzzer:

https://www.tinkercad.com/things/a4hbx2dVWxx-ej3-clase-1-robotica?sharecode=KZhs_Ml-De0m-veg5mNtNY8IWC7tB5Xmol2L_9JPJg8

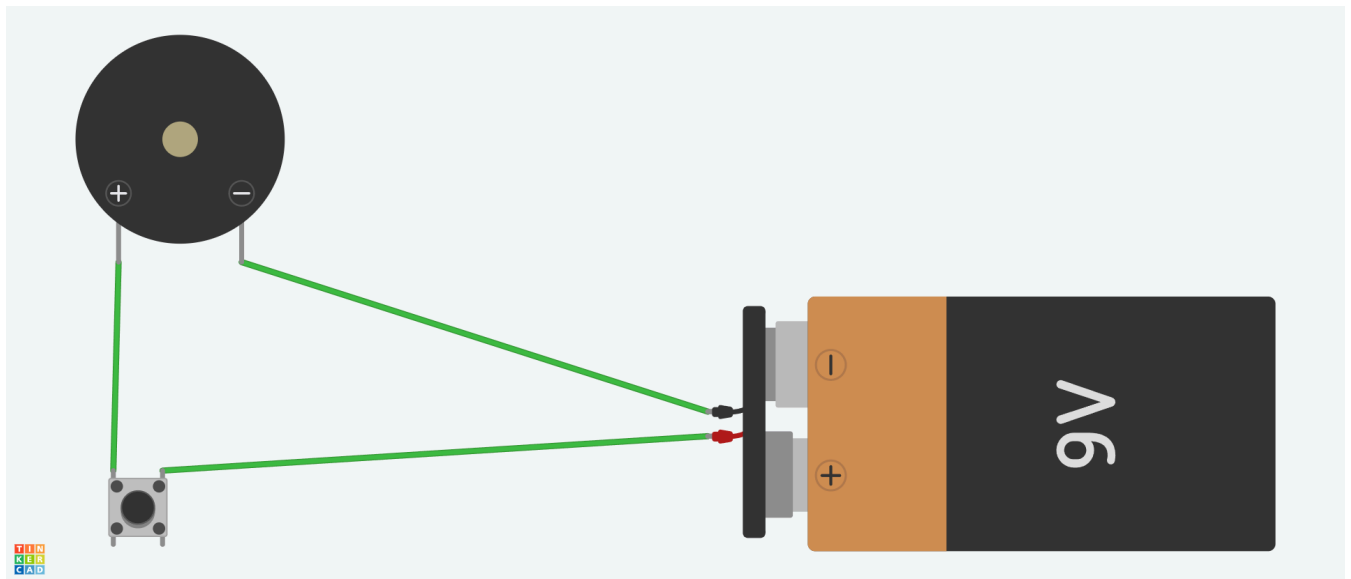

Ejercicio 4 - Switch and Button:


https://www.tinkercad.com/things/dTtOa3oeIEM-ej4-clase-1-robotica?sharecode=85-B2uX8YI4QB8I6QXrsTXwcNHHAc1Qc_efF7jJivjU

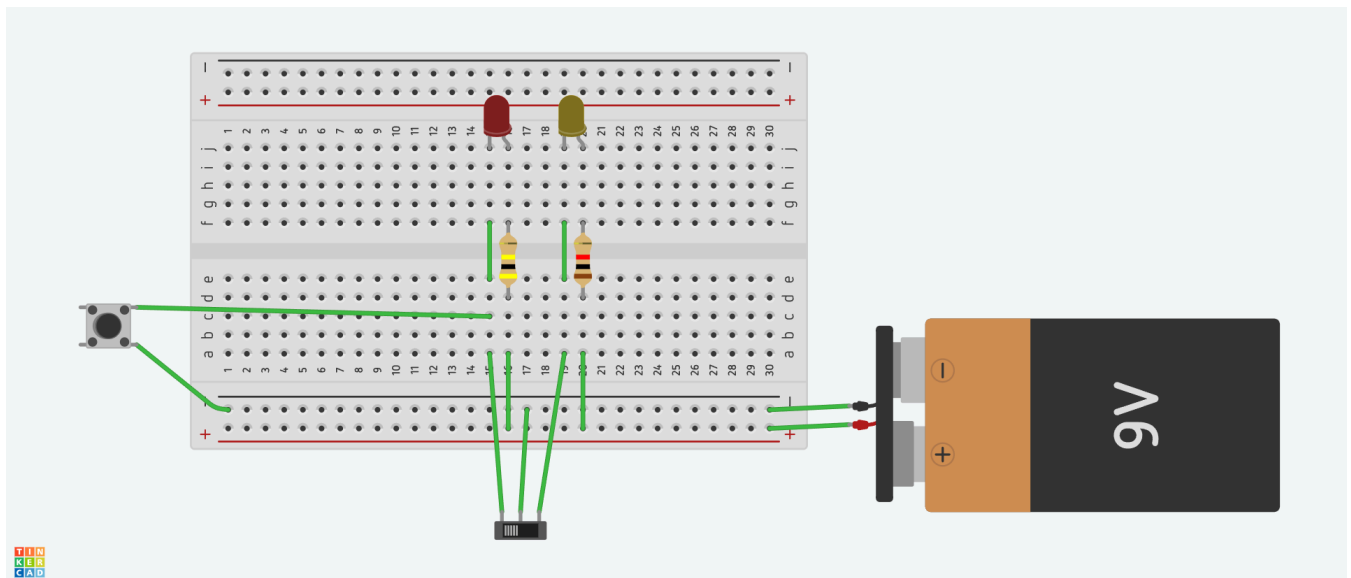

Clase 2


Ejercicio 5 - Transistor npn + led:

<https://www.tinkercad.com/things/eKwabeVFZXJ-ej5-clase-2-robotica?sharecode=pDlwAnOy7yoSL6olgV4lqZpFSh5MojXBiDamtMuEzSM>

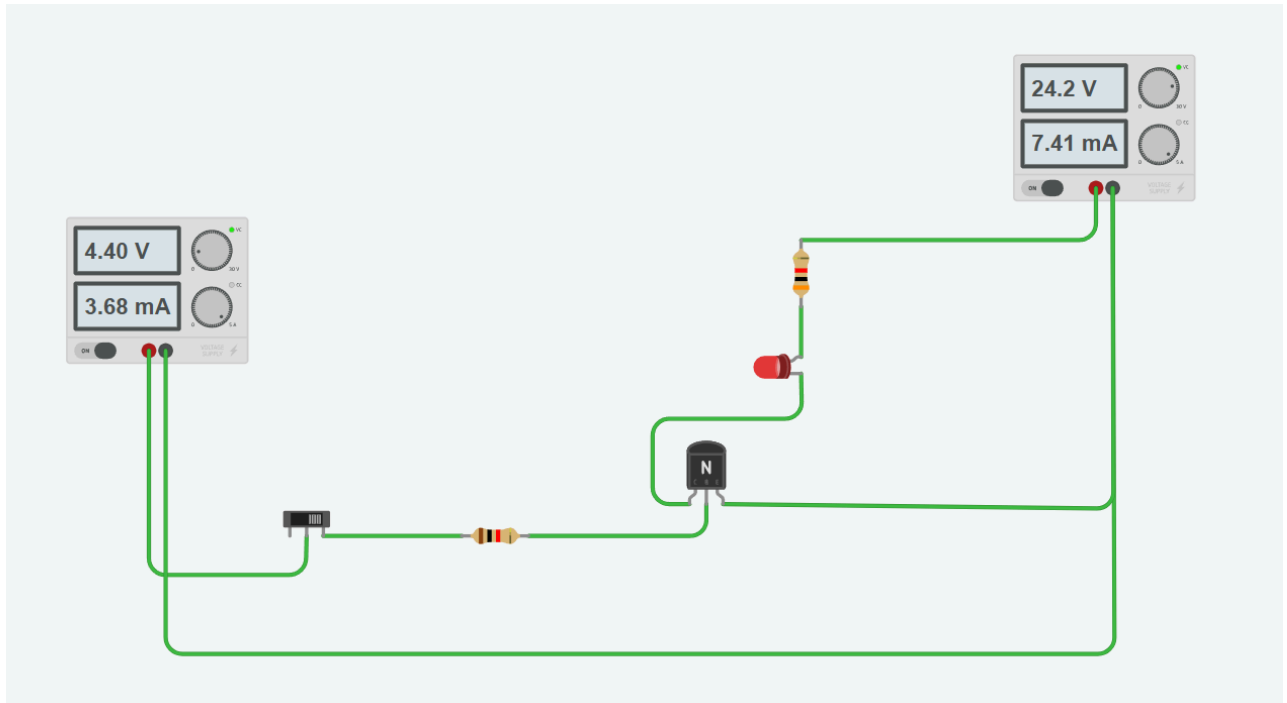


Ejercicio 6 - Osciloscopio en CA:

<https://www.tinkercad.com/things/75eh1D1yzeS-ej6-clase-2-robotica?sharecode=o1QEKabZjvftRKKBLFGgo8CMxutrJH5DQTWkfBnD3iY>

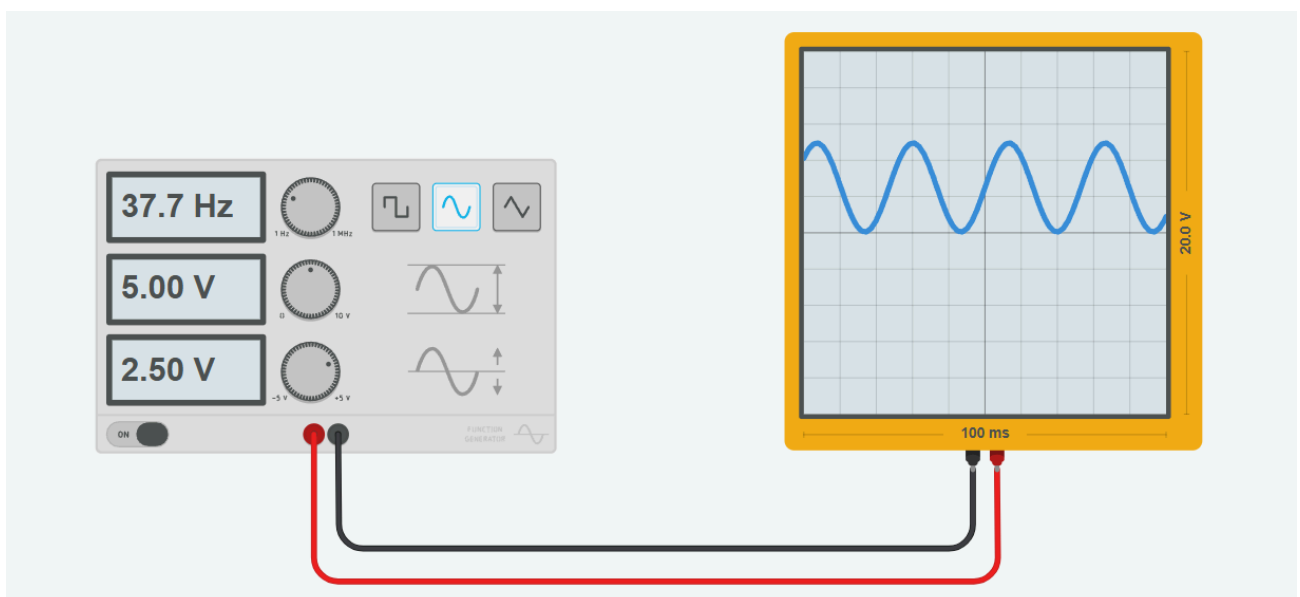


Ejercicio 7 - Osciloscopio señal cuadrada:

<https://www.tinkercad.com/things/75eh1D1yzeS-ej6-clase-2-robotica?sharecode=o1QEKabZjvftRKKBLFGgo8CMxutrJH5DQTWkfBnD3iY>

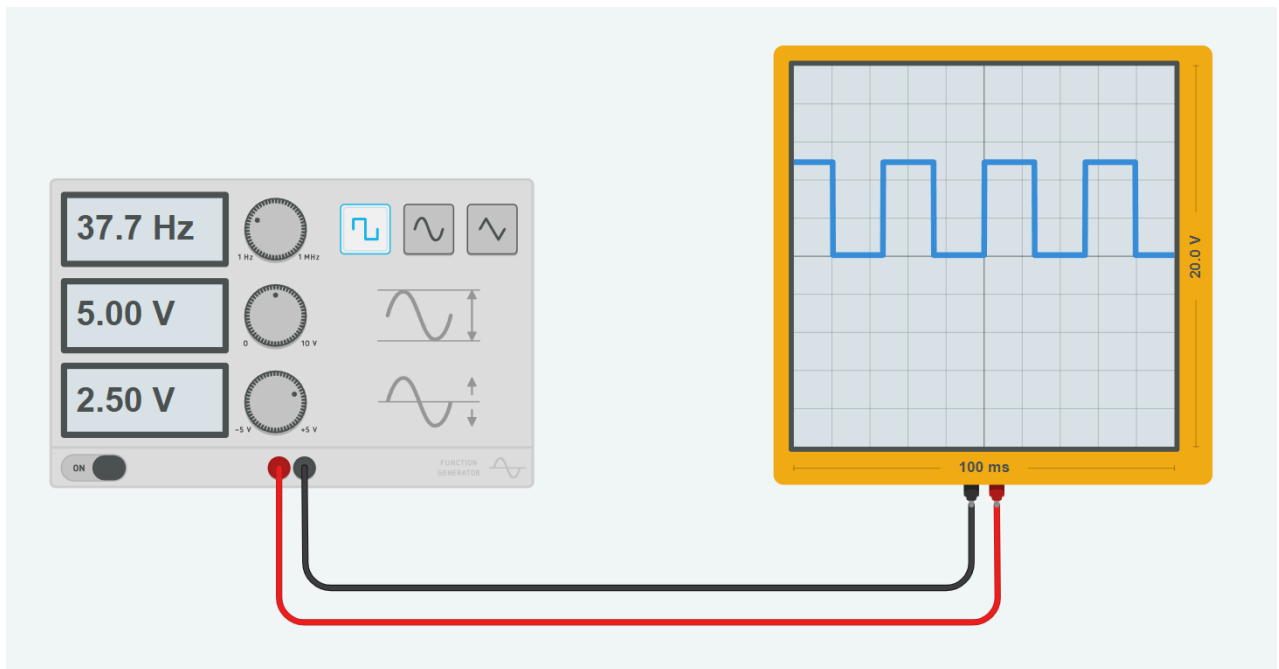

Ejercicio 8 - Fuente rectificadora con puente de diodo:

<https://www.tinkercad.com/things/5wW0mLMpFda-ej8-clase-x-robotica?sharecode=GxUz8X7ZBaSg5alxrFJ9A28aa0fhqWFq3mylDnohl4A>

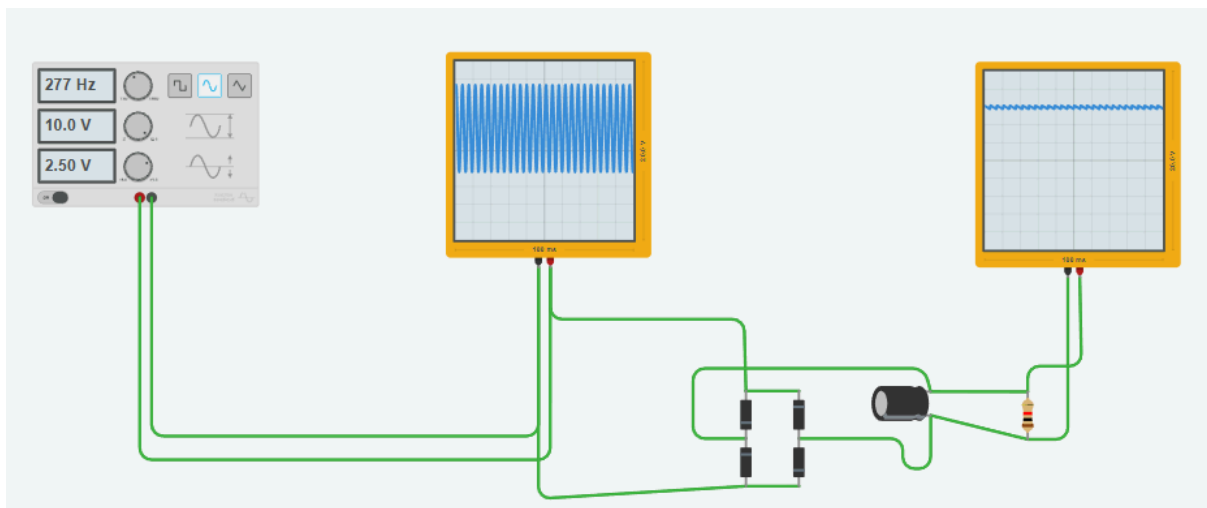

Ejercicio 9 - Tester:

<https://www.tinkercad.com/things/i7C9zmxcsF1-ej9-clase-x-robotica?sharecode=TRZUVgErw3LrfdXATkHwvqeKW4zZZPETzm8Pxr4Swrg>

